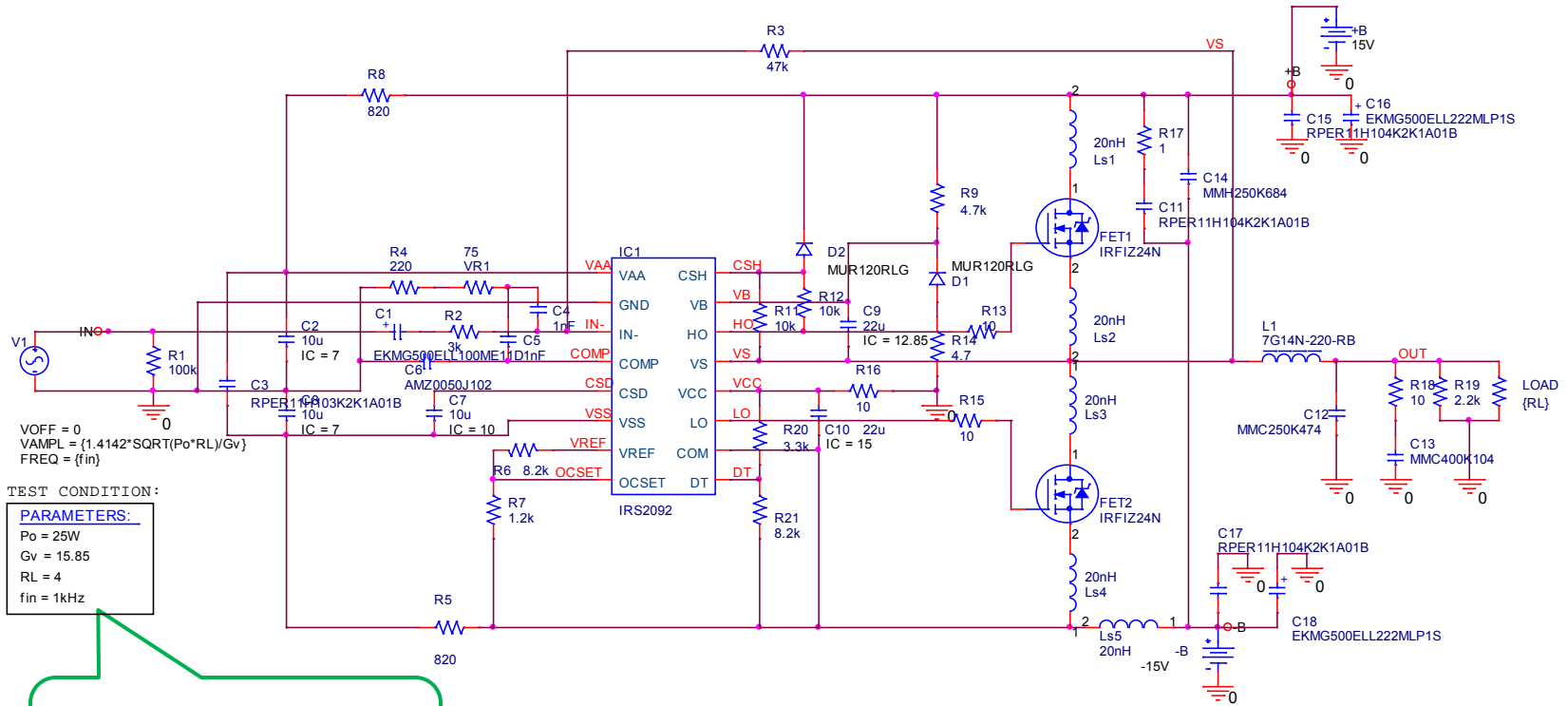




# Specifications : Efficiency Evaluation Circuit



Condition :  
 $P_o = 25[W]$ ,  $4\Omega$  Load

## Analysis

Time Domain (Transient)

Run to time: 3ms

Start saving data after: 1ms

Maximum step size: 100n

Skip the initial transient bias point calculation (SKIPBP)

## .Options

RELTOL: 0.01

VNTOL: 1.0u

ABSTOL: 1.0n

CHGTOL: 0.01p


GMIN: 1.0E-12

ITL1: 500

ITL2: 200


ITL4: 10
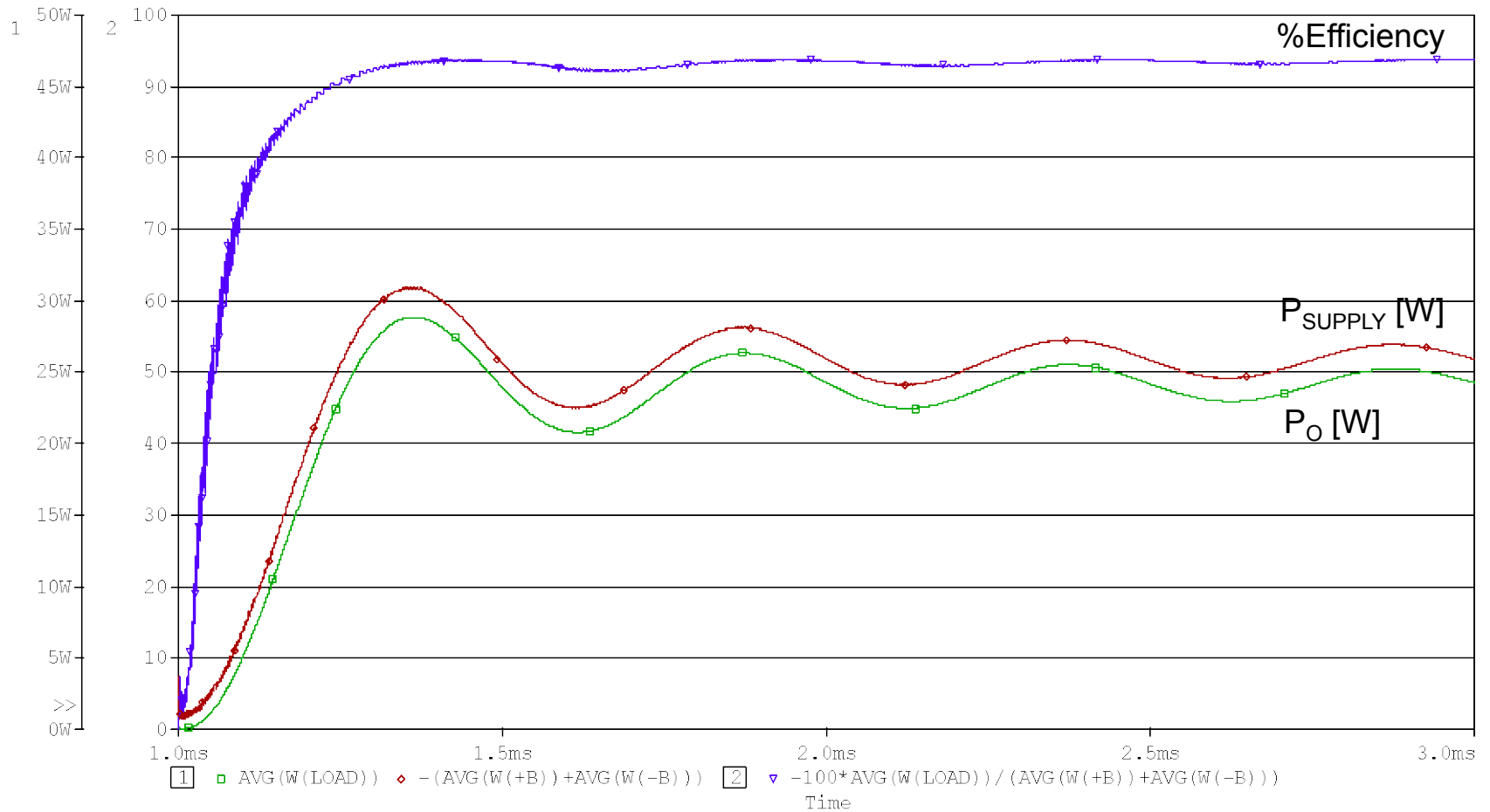
# Specifications : Efficiency Simulation Result


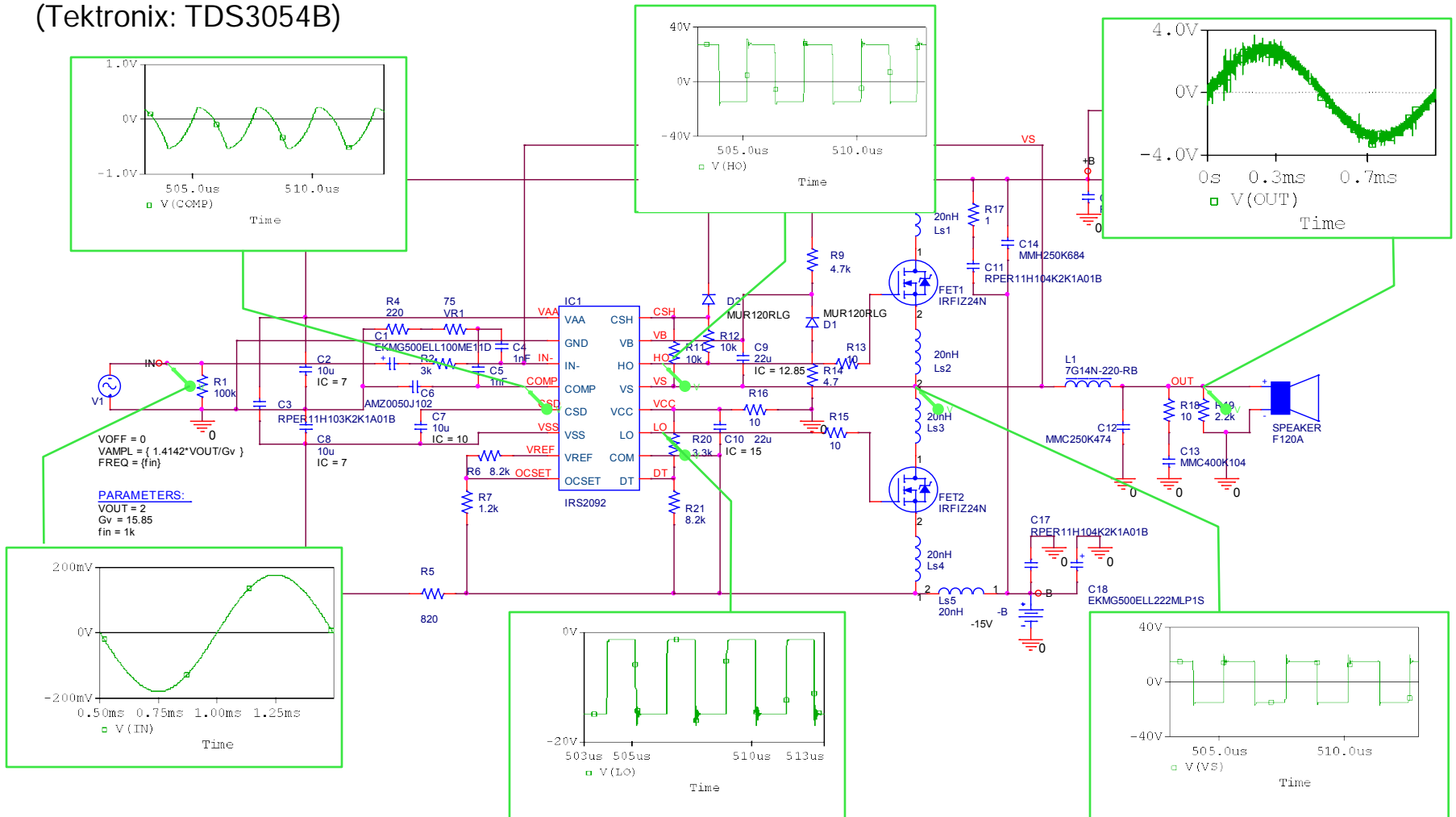
# Waveforms Evaluation


Class D amplifier circuit are simulated and compared with measured waveforms from oscilloscope (Tektronix: TDS3054B)




# Simulated vs. Measured Waveform

OUT



Simulated

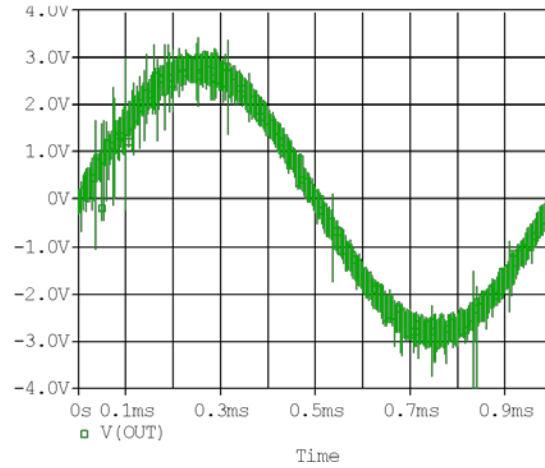

Measured

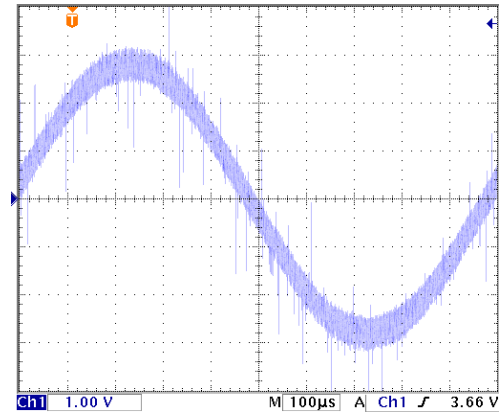


VS

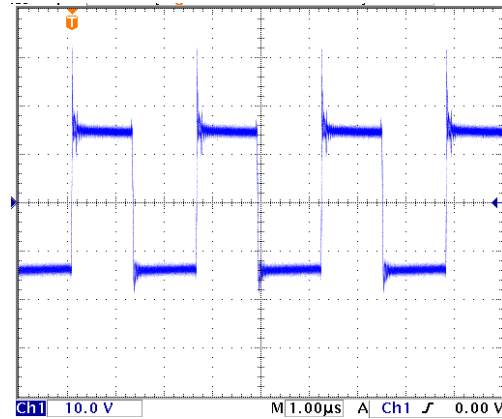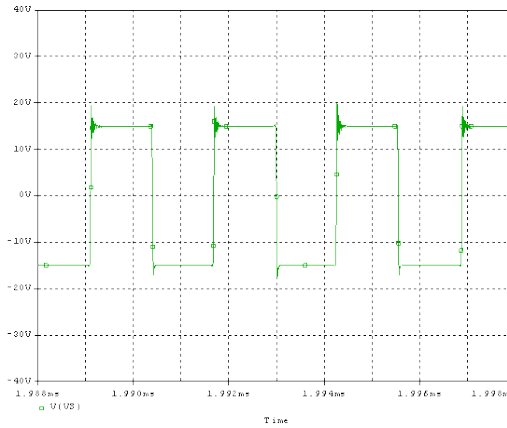


# Self-Oscillating Frequency



Simulated

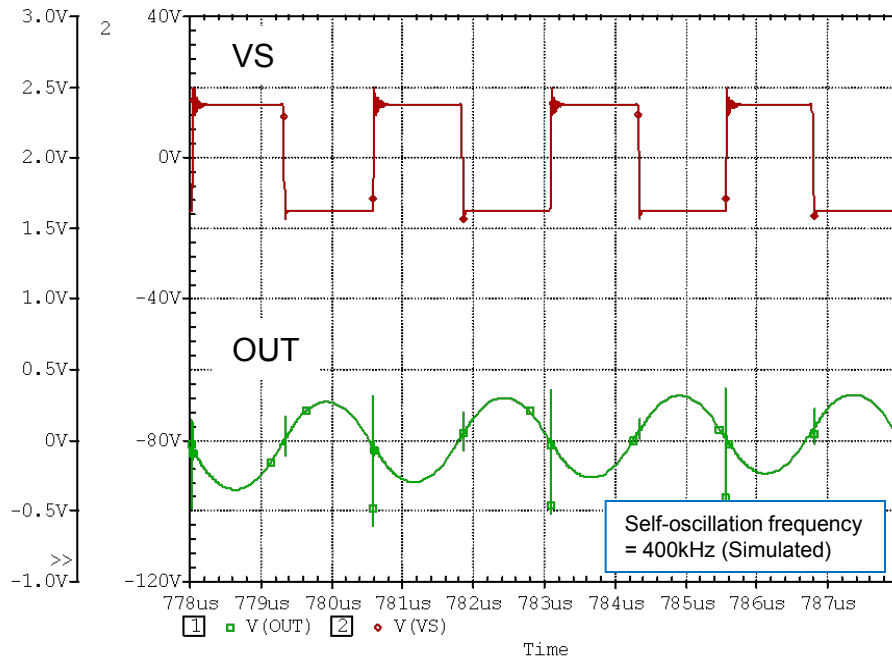

Measured

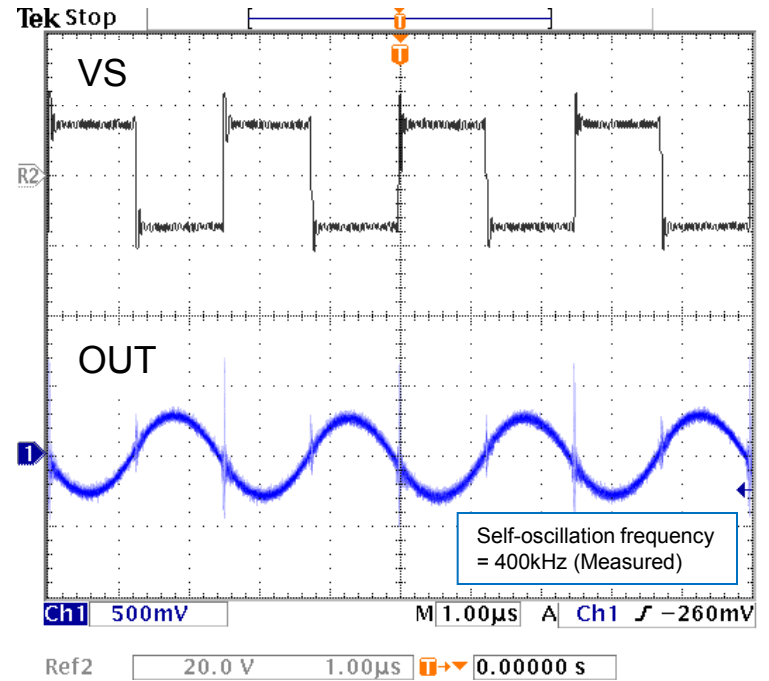

# Dead-time (25ns)

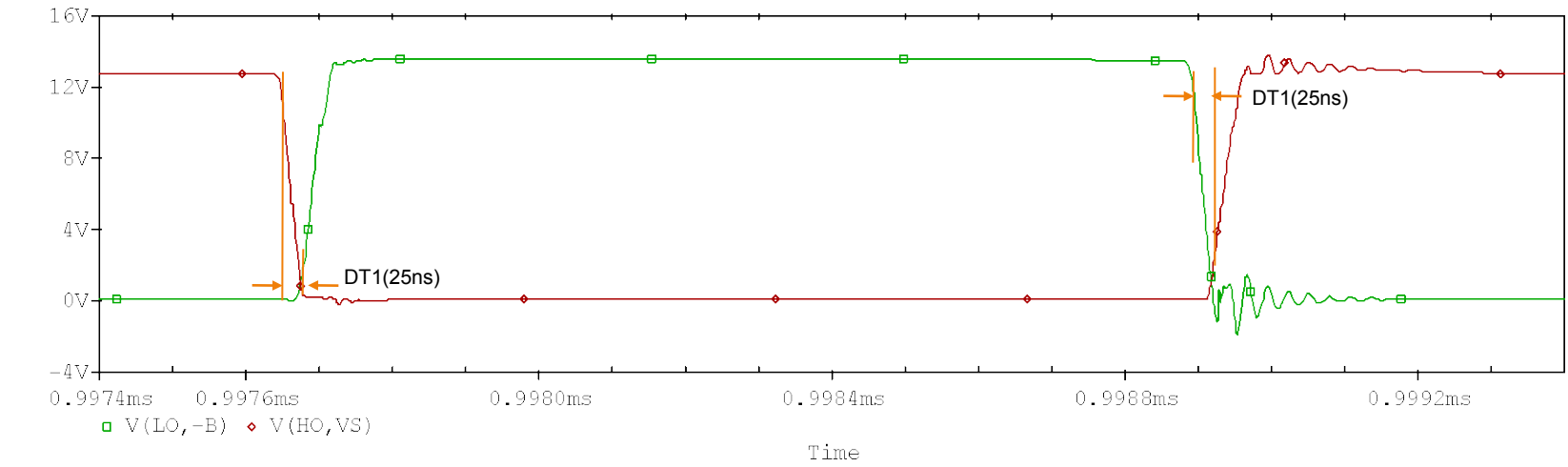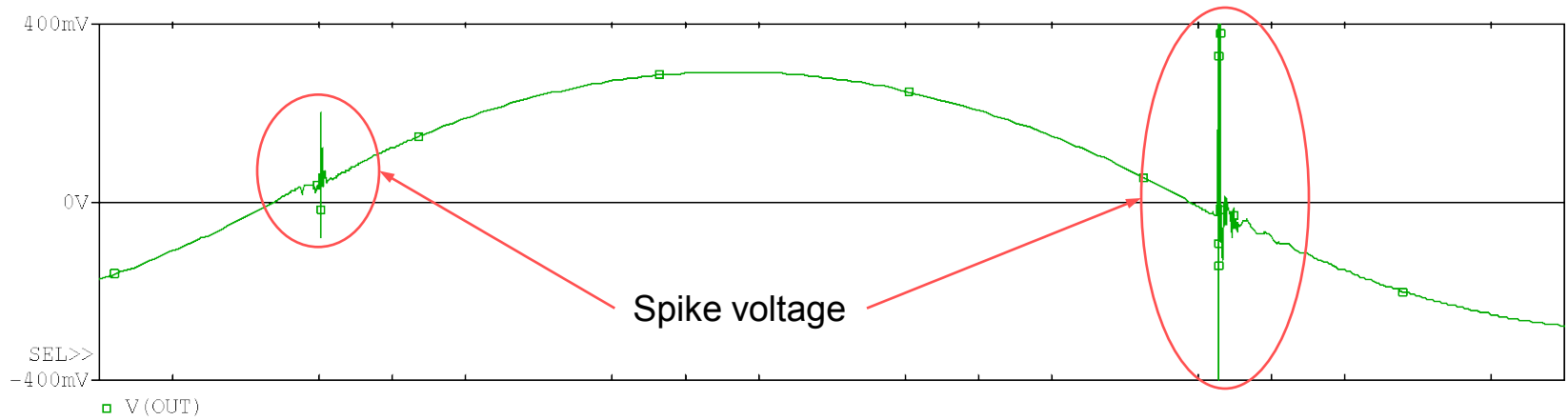

# Power losses FET

FET: ID and VDS are simulated and compared with scope (Tektronix: TDS5054B) waveforms

$P_{SW}$ ,  $P_{cond}$ , and  $P_{gd}$  are calculated by PSpice.

